



Item Navigation

Another Nondimensionalization of the RLC Circuit Equation

Determine how to nondimensionalize the RLC circuit equation so that the dimensionless equation takes the form

$$\alpha \frac{d^2 Q}{d\tau^2} + \frac{dQ}{d\tau} + Q = \cos \beta \tau.$$

What are the definitions of τ , Q , α and β ?

✓ **Completed**

Go to next item



Like



Dislike



Report an issue

